

**DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE**

**Regular & Supplementary Summer – 2023**

**Course: B. Tech. Branch : Electronics and Communication Engineering /**

**Electronics and Telecommunication Engineering**

**Subject Code & Name: Network Theory (BTETC401)**

**Semester : IV**

**Max Marks: 60**

**Date:13/07/2023**


**Duration: 3 Hr.**

**Instructions to the Students:**


1. All the questions are compulsory.
2. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in ( ) in front of the question.
3. Use of non-programmable scientific calculators is allowed.
4. Assume suitable data wherever necessary and mention it clearly.

|                                             |            |           |
|---------------------------------------------|------------|-----------|
|                                             | (Level/CO) | Marks     |
| <b>Q. 1 Solve Any Two of the following.</b> |            | <b>12</b> |


- |                                                                                                           |     |   |
|-----------------------------------------------------------------------------------------------------------|-----|---|
| A) State Kirchhoff's laws and Determine the current through the $5\ \Omega$ resistor of the network shown | CO1 | 6 |
|-----------------------------------------------------------------------------------------------------------|-----|---|

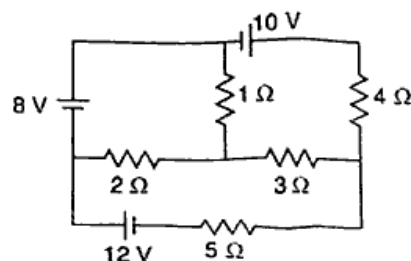

- |                                                                                                                                          |     |   |
|------------------------------------------------------------------------------------------------------------------------------------------|-----|---|
| B) State superposition theorem and find the current passing through the $3\ \Omega$ resistor in the circuit using superposition theorem. | CO1 | 6 |
|------------------------------------------------------------------------------------------------------------------------------------------|-----|---|

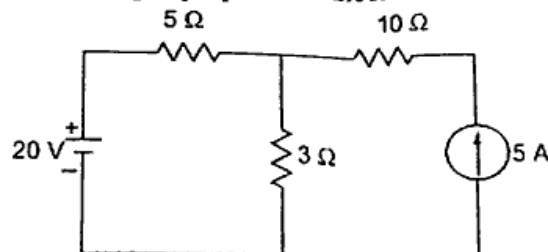


- |                                                                                                                        |     |   |
|------------------------------------------------------------------------------------------------------------------------|-----|---|
| C) The graph of a network is shown in Fig. Write the (a) incidence matrix, (b) tieset matrix, and (c) f-cutset matrix. | CO1 | 6 |
|------------------------------------------------------------------------------------------------------------------------|-----|---|

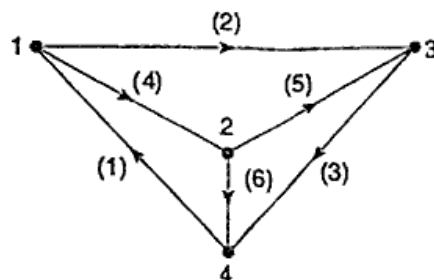


|                                            |  |           |
|--------------------------------------------|--|-----------|
| <b>Q.2 Solve Any Two of the following.</b> |  | <b>12</b> |
|--------------------------------------------|--|-----------|

- |                                                                                                                                                           |          |   |
|-----------------------------------------------------------------------------------------------------------------------------------------------------------|----------|---|
| A) What are initial conditions? Explain the initial conditions for Resistor, capacitor and inductor                                                       | CO1, CO3 | 6 |
| B) In the given network of Fig., the switch is closed at $t = 0$ . With zero current in the inductor, find $i$ , $di/dt$ and $d^2 i / dt^2$ at $t = 0+$ . | CO1, CO3 | 6 |

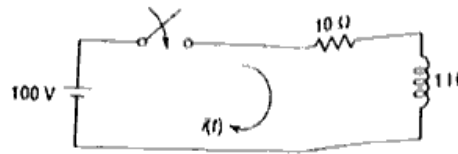

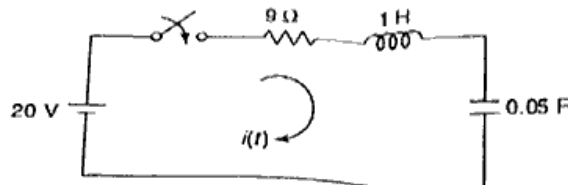- C) In the network of Fig. shown, the switch is closed at  $t = 0$ . Obtain the expression for current  $i(t)$  (use time domain approach) CO1, CO3 6




**Q. 3 Solve Any Two of the following.**

12

- A) In the network of Fig. 7.12, the switch is moved from the position 1 to 2 at  $t = 0$ , steady-state condition having been established in the position 1. Determine  $i(t)$  for  $t > 0$  (Using S-domain)

CO1 6

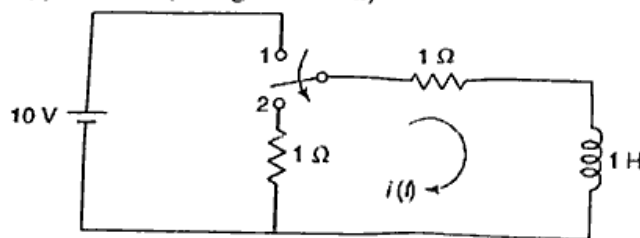

- B) To find Initial and Final values if they exist of the signal with L.T.

CO1 6

$$(a) F(s) = \frac{7s^2 + 63s + 134}{(s+3)(s+4)(s+5)} \quad (b) F(s) = \frac{4s^2 + 7s + 1}{s(s+1)^2}$$

$$(c) F(s) = \frac{40}{(s^2 + 4s + 5)^2}$$

- C) Find Laplace Transform of various standard time domain functions


CO1 6

**Q.4 Solve Any Two of the following.**

12

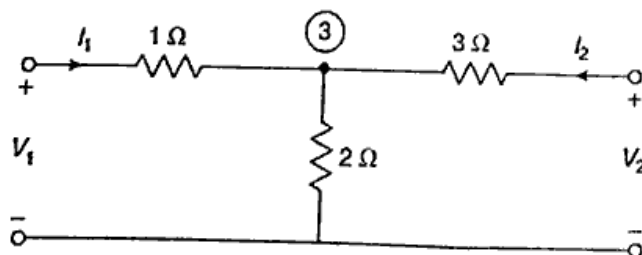
- A) Define the terms: Driving-point Impedance Function, Driving-point Admittance Function CO1, CO4 6

Find Y-parameters for the network shown in Fig



- B) Derive h-parameter in terms of Z parameter, Y-parameter and ABCD parameter CO1, CO4 6

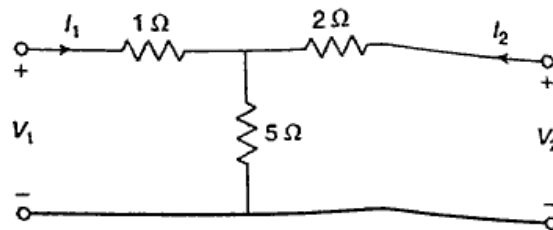- C) Find the transmission or general circuit parameters for the circuit shown in Fig. Comment on reciprocity and symmetry CO1, CO4 6




**Q. 5 Solve Any Two of the following.**

**12**

- A) Explain about classification of filters. Draw the characteristics of Low-pass and High-pass filters. CO1, CO3 6
- B) Realise the following function in Foster-I and Foster-II forms CO1, CO3 6

$$Z(s) = \frac{3(s+2)(s+4)}{s(s+3)}$$

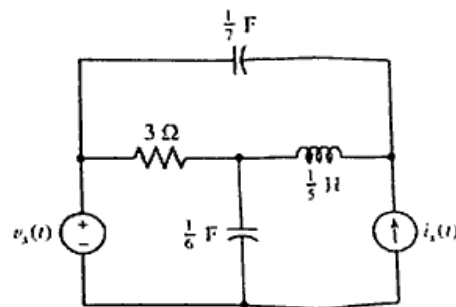- C) Obtain the normal-form equations for the circuit of Fig. shown, a four-node circuit containing two capacitors, one inductor, and two independent sources CO1, CO3 6



\*\*\* End \*\*\*