

DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE
End Semester Examination – Winter 2018

Course: B. Tech in Electrical Engineering
Subject Name: Network Analysis and Synthesis
Date: 03/12/2018

Max Marks: 60

Semester: III
Subject Code: BTEEC302
Duration: 3 Hrs.

Instructions to the Students:


1. Solve **ANY FIVE** questions out of the following.
2. Students should note, no supplement will be provided.
3. Use of non-programmable scientific calculators is allowed.
4. Assume suitable data wherever necessary and mention it clearly.

Marks

Q. 1 Solve Any Two sub questions

- A) Use superposition theorem to find current through branch A-B in the Circuit of figure

06

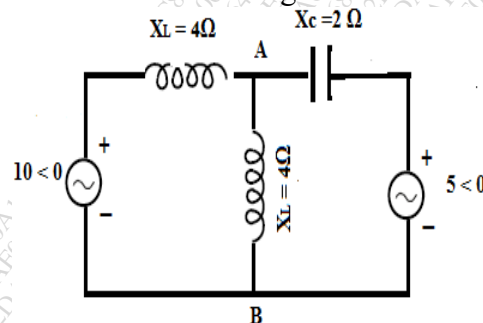

- B) Explain the following terms:
i) Independent and Dependent sources.
ii) Lumped and distributed systems.

06


- C) State and Explain maximum Power transfer theorem in case A.C circuits

06

Q.2 Solve Any Two sub questions


- A) Using Nodal Analysis find Voltage ' V_y ' for given N/W

06

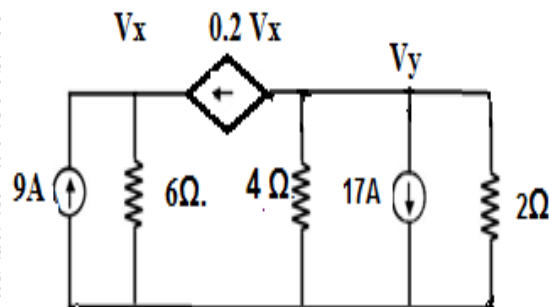

B) Obtain dual network for the circuit given below

06

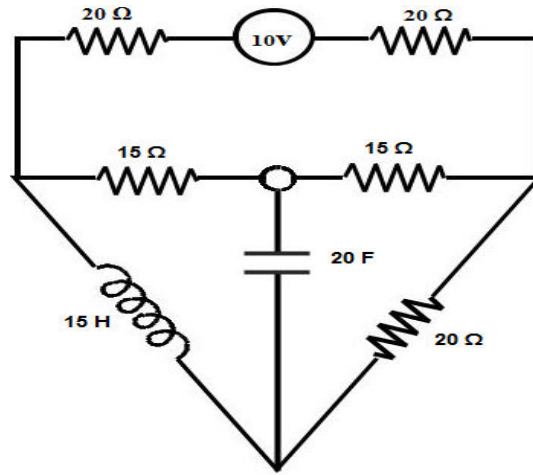

C) Define the following

06

- i. Planner graph ii. NonPlanner graph
- iii. Subgraph. iv. Tree and Co-Tree


Q. 3 Solve All Sub-Questions

A) Explain response of RL series circuit to D.C. excitation

06

B) Find the expression of current when 50V dc source is applied as switch K is opened At $t=0$,


06

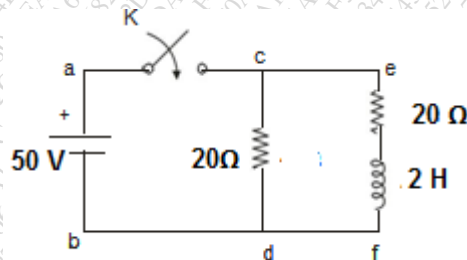

Q.4 Solve All Sub-Questions

A) Find the Laplace transform of the waveform

06

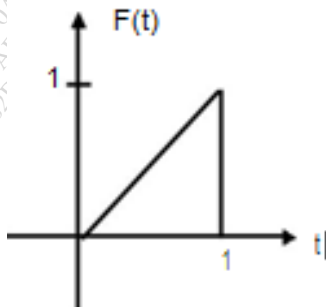


B) Explain Concept of Complex Frequency in detail

06

Q. 5 Solve All Sub-Questions

A) Determine the Open circuit parameters for the circuit shown below

06

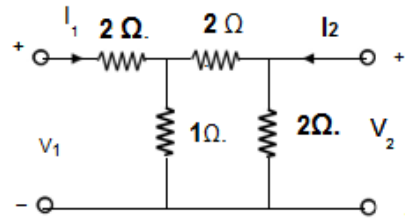

B) What is the physical significance of Pole and Zero in a transfer function?

06

Q. 6 Solve All Sub-Questions

A) What is Meant by Resonance in RLC Series Circuit and Derive equation for resonant Frequency

06

B) Explain the High pass filter and band pass filter.

04

C) A Coil of inductance 31.8mH and resistance of 10Ω is connected in parallel across 250V,50Hz. Determine value of Capacitance so that total current is in phase supply voltage

02

*** End ***