

C)	Draw the block diagram & circuit of SIPO shift register and explain its working.	CO4	6
Q. 5	Solve Any Two of the following.		12
A)	Minimize the following expression and realize using basic gates $Y = \sum m (0,2,5,6,7,8,10,13,15)$	CO5	6
B)	State working principle of de-multiplexer. Explain 1 to 8 line demultiplexer with a neat diagram.?	CO5	6
C)	Draw a block diagram of full adder. Write a truth table. Draw logic diagram of it?	CO5	6
*** End ***			

The grid and the borders of the table will be hidden before final printing.