

DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE

Regular/Supplementary Winter Examination – 2024

Course: B.Tech

Branch : Electrical Engineering / Electrical Engineering
(Electronics and Power)/ Electrical & Electronics Engg.

/ Electrical & Power

Subject Code & Name: BTEEC303 Electrical and Electronics Measurement

Max Marks: 60

Semester: III

Date: 10/02/2025

Duration: 3 Hr.

Instructions to the Students:

1. Each question carries 12 marks.
2. Question No. 1 will be compulsory and include objective-type questions.
3. Candidates are required to attempt any four questions from Question No. 2 to Question No. 6.
4. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in () in front of the question.
5. Use of non-programmable scientific calculators is allowed.
6. Assume suitable data wherever necessary and mention it clearly.

Q. 1 Objective type questions. (Compulsory Question)

Level/CO Marks

- | | | |
|---------------------------------|--|----|
| 1 | smallest change in a measured variable to which an instrument will respond is: | 12 |
| a) Accuracy | b) Resolution | 1 |
| c) Precision | d) drift | |
| 2 | The difference between the indicated value and the true value of a quantity is : | 1 |
| a) gross error | b) dynamic error | |
| c) absolute error | d) relative error | |
| 3 | If the instrument has square law response, it can be used for the instrument of: | 1 |
| a) DC voltage only | b) AC voltage & current | |
| c) Both AC and DC quantities | d) Resistance only | |
| 4 | The primary current in CT is detected by: | 1 |
| a) Secondary burden | b) core of transformer | |
| c) load current | d) none of the above | |
| 5 | The Wheatstone bridge method of resistance measurement is ideally suitable for the | 1 |
| a) 0.001Ω to 1Ω | b) 0.1Ω to 100Ω | |
| c) 100Ω to $10 K\Omega$ | d) $100 k\Omega$ to $10 M\Omega$ | |
| 6 | Schering bridge can be used to measure which one of the followings: | 1 |
| a) Inductance | b) Resistance | |
| c) Capacitance | d) Power | |
| 7 | Which bridge measures self-inductance using a standard capacitor? | 1 |
| a) Maxwell bridge | b) Schering bridge | |
| c) Anderson bridge | d) Wien bridge | |

- 8 A digital storage oscilloscope (DSO) is used to .
- | | | | |
|--------------------------------|--------------------------------|--|----------------------------------|
| a) Generate sinusoidal signals | b) Measure instantaneous power | c) Store and analyze waveforms digitally | d) Measure electrical resistance |
|--------------------------------|--------------------------------|--|----------------------------------|
- 9 Which transducer is commonly used for temperature measurement?
- | | | | |
|---------|-----------------|---------|-----------------|
| a) RVDT | b) Thermocouple | c) LVDT | d) Strain gauge |
|---------|-----------------|---------|-----------------|
- 10 Which of the following is NOT a type of transducer?
- | | | | |
|---------------|---------|-----------------------|-----------------|
| a) Thermistor | b) LVDT | c) Hall effect sensor | d) Oscilloscope |
|---------------|---------|-----------------------|-----------------|
- 11 Which characteristic is crucial for selecting a transducer?
- | | | | |
|---------------|----------------|---------|---------|
| a) Durability | b) Sensitivity | c) Size | d) Cost |
|---------------|----------------|---------|---------|
- 12 Signal conditioning is essential for:
- | | | | |
|-----------------------------|--|--------------------------------|----------------------------------|
| a) Direct data transmission | b) Converting raw signals into a usable format | c) Measuring mechanical stress | d) Storing large amounts of data |
|-----------------------------|--|--------------------------------|----------------------------------|

Q. 2 Solve the following.

- A)** Define error. Explain the different types of errors with example.
- B)** Describe the characteristics of instruments & measurement system.

Q. 3 Solve the following.

- A)** Draw neat sketch of PMMC instrument and derive the equation and explain in detail.
- B)** Explain two wattmeter method for measurement of power in three phase circuit.

Q. 4 Solve Any Two of the following.

- A)** The inductance of moving iron ammeter is given by following expression $L = (20 + 10\theta - 2\theta^2) \mu H$, where, θ is deflection in radians. The spring constant is 24×10^{-6} Nm/rad. Calculate the values of deflection for a current 5A.
- B)** With neat, labeled diagram explain Maxwell's Inductance bridge and obtain the output equation for L_x and R_x .
- C)** With a circuit & phasor diagram derive the equation for an unknown self-inductance measurement using HAY'S bridge.

Q. 5 Solve Any Two of the following.

- A)** Explain the working of Q Meter.
- B)** Draw and explain Ramp type DVM in detail.
- C)** Explain in detail the construction and working of digital storage oscilloscope.

Q.6 Solve Any Two of the following.

- A) Explain the working of strain gauge in detail.**
- B) Explain different characteristics of transducer.**
- C) With a neat, labeled diagram explain the operation of LVDT.**

CO1	6
CO2	6
CO3	6

12

***** End *****

22823138

22823138

22823138

22823138

22823138

22823138

22823138

22823138

22823138