

Course: B. Tech.

Branch: Elect. & Instrumentation Semester :VIIIth

Subject Code & Name: BTEIEP801:4 DC POWER TRANSMISSION SYSTEMS

Max Marks: 60

Date:07/07/2022

Duration: 3.45 Hr.

Instructions to the Students:

1. All the questions are compulsory.
2. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in () in front of the question.
3. Use of non-programmable scientific calculators is allowed.
4. Assume suitable data wherever necessary and mention it clearly.

(Level/CO) Marks

Q. 1 Solve Any Six of the following.

12

- A) What are the requirements for the choice of converter configuration?
- B) Define pulse number?
- C) What is valve utilization factor?
- D) State TUF meaning
- E) Why the necessity of control in a DC link?
- F) Define current margin
- G) Draw the circuit of Graetz circuit.

Q.2 Solve Any Three of the following.

12

- A) Write the advantages and disadvantages of HVDC Transmission Advantages
- B) Explain **Thyristors-based LCCs** Technology.
- C) State differences between LCC and CCC
- D) Explain Commutation margin angle of 6 pulse LCC

Q. 3 Solve Any One of the following.

6

- A) Draw and Explain schematic diagram of a12 pulse LCC circuit.
- B) Explain Link commutated Converter.

Q.4 Solve Any Two of the following.

20

- A) Draw and Explain HVDC Converter Station.
- B) State and Explain different types of HVDC links.
- C) Explain Converter control characteristics.

Q. 5 Write a short note on the following.

10

- A) Double tuned and damped filters.
- B) Reactive power requirement

*** End ***