

DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE

END-SEM EXAMINATION- Summer 2019

Course: B. Tech in Electronics and Telecommunication Engineering

Sem: III

Subject Name: Network Analysis

Subject Code: BETX304

Max Marks: 60


Date: 31/05/2019

Duration: 3 Hr.

Instructions to the Students:

1. Solve **ANY FIVE** questions out of the following.
2. The level question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in () in front of the question.
3. Use of non-programmable scientific calculators is allowed.
4. Assume suitable data wherever necessary and mention it clearly.


	(Level/CO)	Marks
Q.1 Solve the following.	CO01	
A) Explain the terms		[06]
(a) Passive network and active network		
(b) Linear Element and Nonlinear element		
(c) Lumped Element and distributed element		
B) With the help of mesh analysis find current through $6\ \Omega$ capacitor show in figure.		[06]

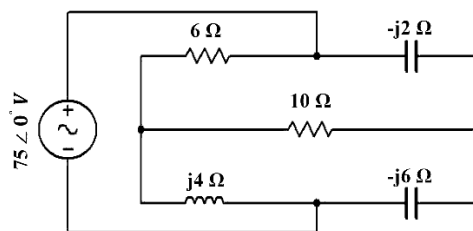


Q.2 Solve.	CO02	
A) Derive expression for frequencies at which voltage across L and C are maximum in series resonant circuit.		[08]
B) A series RLC circuit with resistance of $10\ \Omega$ inductance of $0.2\ \text{H}$ and capacitance of $100\ \mu\text{F}$ is applied by voltage source of $50\ \text{V}$. Find resonant frequency.		[04]
Q.3 Solve any one the following.		
A) Design a composite high pass filter to operate into load of $600\ \Omega$ and have cutoff frequency of $1.6\ \text{kHz}$. The filter should on constant k section, one m derived section with frequency of infinite attenuation is $1.3\ \text{kHz}$ and a suitable termination half section.		[12]
B) I) Define characteristic impedance. Derive and expression for characteristic impedance of symmetrical T network in terms of open and short circuit impedances.		[06]
II) Design a prototype high pass filter section if design impedance $R_0 = 300\ \Omega$ and cut off frequency (a) $f_c = 100\ \text{Hz}$, (b) $f_c = 200\ \text{Hz}$.		[06]

Q.4 Solve any two of the following.**CO01**

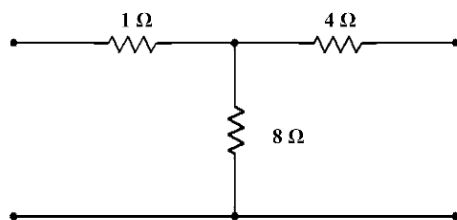
- A) Define: (a) forward transfer admittance, (b) forward transfer impedance, (c) voltage transfer ratio and (d) current transfer ratio. [06]
- B) For the network shown below determine ABCD (transmission) parameter. [06]



- C) For the network shown below determine Y (short circuit admittance) parameter. [06]
Also verify condition for reciprocity and symmetry for the same.

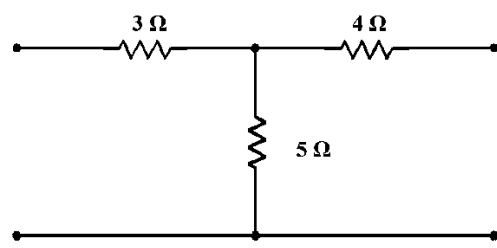**Q.5 Solve the following.****CO01,CO03**

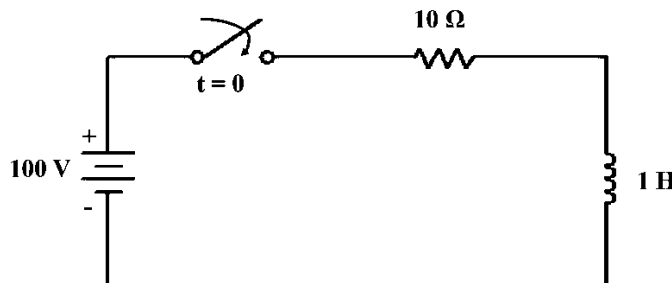- A) The switch is closed at $t = 0$ find value of i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$. Assume initial current in the inductor to be zero. [06]



- B) Explain behavior of basic elements (R, L and C) in Laplace domain. [06]

Q.6 Solve any two of the following**CO03,CO04**

- A) Explain in brief: (a) types of transmission lines and (b) parameters of transmission line. [06]
- B) What is distortion less line? Derive the condition for a distortion less transmission line. [06]
- C) a transmission line has following parameters at 1 kHz frequency
 $R = 4 \Omega/\text{km}$, $L = 1 \text{ mH}/\text{km}$, $G = 0.5 \times 10^{-6} \text{ mho}/\text{km}$ and $C = 0.001 \mu\text{F}/\text{km}$. Calculate Z_0 , attenuation constant, phase constant, wavelength, phase velocity. [06]

***** End *****